

**P1 - Ch18 (30%) [Electric force/field]**

- a)  $q_1 = q_2 = q_3 = q_4 = 10 \mu\text{C}$  in Fig. 1. Find the electric force exerted on  $q_3$ , Mag. 957 N, Dir. y
- b)  $Q_1 = Q_2 = 20 \mu\text{C}$  in Fig. 2. Find the electric field at point  $P_1$ , Mag.  $1.4\text{E}8 \text{ N/C}$ , Dir. y
- c) If  $Q_1 = -10 \mu\text{C}$ ,  $Q_2 = 10 \mu\text{C}$  in Fig. 2. Recalculate electric field at  $P_1$ , Mag.  $7.0\text{E}7 \text{ N/C}$ , Dir. -x

Fig. 1


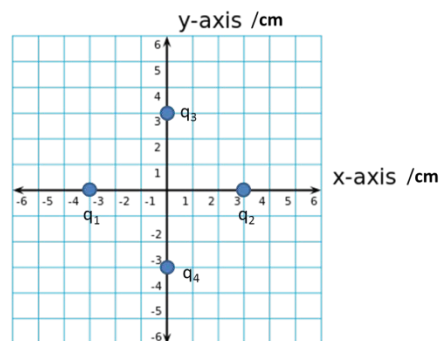


Fig. 2

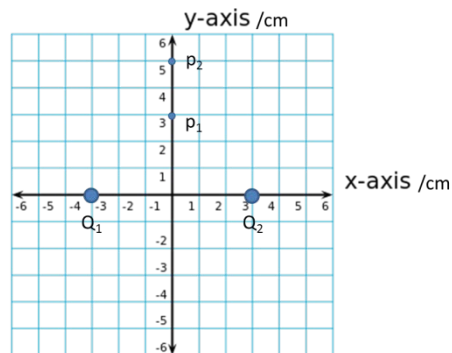

**P2 - Ch19 (20%) [Electric potential/potential energy]**

- a) In Fig.2,  $Q_1 = Q_2 = 20 \mu\text{C}$ , find the electric potential at  $P_1$ . Ans.  $8.5\text{E}6 \text{ V}$
- b) Find the electric potential at  $P_2$ . Ans.  $6.2\text{E}6 \text{ V}$
- c) Find the work needed to move a point charge  $q = 25 \mu\text{C}$  from point  $P_2$  to  $P_1$ . Ans.  $57.5 \text{ J}$
- d) If a point charge  $q = 25 \mu\text{C}$  is placed at  $P_1$ , what is the electric potential energy of this charge? Ans.  $212.5 \text{ J}$

**P3- Ch19 (25%) [Capacitors]**

- a) In Fig. 3,  $C_1 = 10 \mu\text{F}$ ,  $C_2 = C_3 = 5 \mu\text{F}$ . Find the total capacitance connected to the 9-V battery. Ans.  $5 \mu\text{F}$
- b) Find the voltage on  $C_2$ . Ans.  $4.5 \text{ V}$
- c) Find the charge on  $C_1$ . Ans.  $45 \mu\text{C}$
- d) Find the electric energy stored on  $C_1$ . Ans.  $101 \mu\text{J}$
- e) Find the current passing through the battery at equilibrium. Ans. 0

Fig. 3


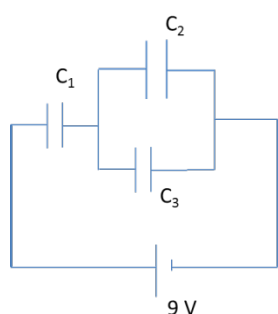


Fig. 4

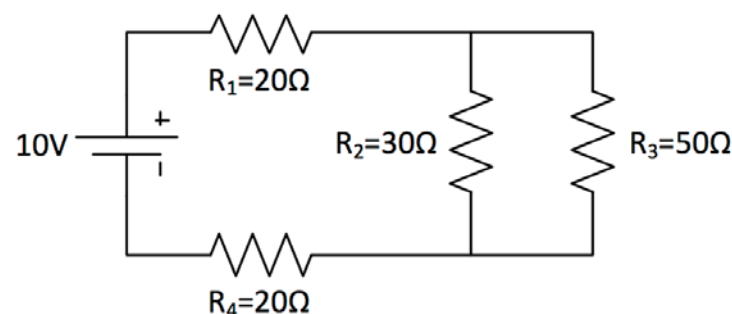

**P4 - Ch21 (25%) [Ohm's law, power]**

- a) In Fig. 4, what is the current in  $R_1$ ? Ans.  $0.17 \text{ A}$
- b) The current in  $R_2$ ? Ans.  $0.11 \text{ A}$
- c) The current on  $R_3$ ? Ans.  $0.06 \text{ A}$
- d) The voltage on  $R_4$ ? Ans.  $3.4 \text{ V}$ ; e) the electric power on  $R_4$ ? Ans.  $0.58 \text{ W}$