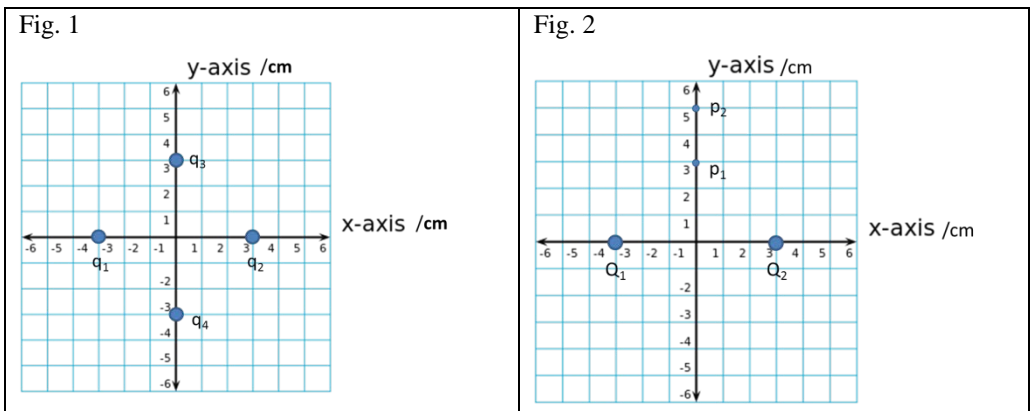


**P1 - Ch18 (30%) [Electric force/field]**

- a)  $q_1 = q_2 = q_3 = q_4 = 20 \mu\text{C}$  in Fig. 1. Find the electric force exerted on  $q_3$ , Mag. 3838 N, Dir. \_\_\_\_\_ y \_\_\_\_\_
- b)  $Q_1 = Q_2 = 20 \mu\text{C}$  in Fig. 2. Find the electric field at point  $P_1$ , Mag. 1.4E8 N/C, Dir. \_\_\_\_\_ y \_\_\_\_\_
- c) If  $Q_1 = -10 \mu\text{C}$ ,  $Q_2 = 10 \mu\text{C}$  in Fig. 2. Recalculate electric field at  $P_1$ , Mag. 7E7 N/C, Dir. \_\_\_\_\_ - x \_\_\_\_\_




**P2 - Ch19 (20%) [Electric potential/potential energy]**

- a) In Fig.2,  $Q_1 = Q_2 = 40 \mu\text{C}$ , find the electric potential at  $P_1$ . Ans. 1.7E7 V \_\_\_\_\_
- b) Find the electric potential at  $P_2$ . Ans. 1.24E7 V \_\_\_\_\_
- c) Find the work needed to move a point charge  $q = 25 \mu\text{C}$  from point  $P_2$  to  $P_1$ . Ans. 115 J \_\_\_\_\_
- d) If a point charge  $q = 25 \mu\text{C}$  is placed at  $P_1$ , what is the electric potential energy of this charge? Ans. 425 J \_\_\_\_\_

**P3- Ch19 (25%) [Capacitors]**

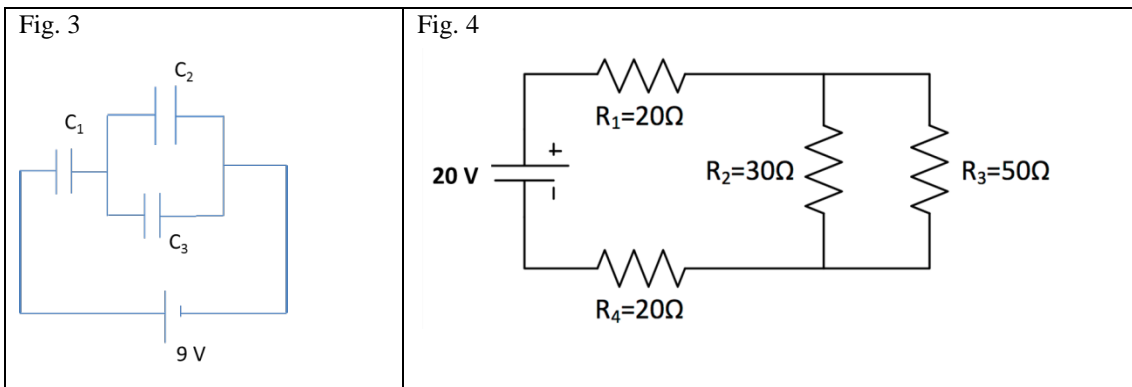- a) In Fig. 3,  $C_1 = 40 \mu\text{F}$ ,  $C_2 = C_3 = 20 \mu\text{F}$ . Find the total capacitance connected to the 9-V battery. Ans. 20 uF \_\_\_\_\_
- b) Find the voltage on  $C_2$ , Ans. 4.5 V \_\_\_\_\_
- c) Find the charge on  $C_1$ , Ans. 180 uC \_\_\_\_\_
- d) Find the electric energy stored on  $C_1$ , Ans. 405 uJ \_\_\_\_\_
- e) Find the current passing through the battery at equilibrium. Ans. 0 \_\_\_\_\_



**P4 - Ch21 (25%) [Ohm's law, power]**

- a) In Fig. 4, what is the current in  $R_1$ ? Ans. 0.34 A \_\_\_\_\_
- b) The current in  $R_2$ ? Ans. 0.21 A \_\_\_\_\_
- c) The current on  $R_3$ ? Ans. 0.13 A \_\_\_\_\_
- d) The voltage on  $R_4$ ? Ans. 6.8 V \_\_\_\_\_; e) the electric power on  $R_4$ ? Ans. 2.31 W \_\_\_\_\_