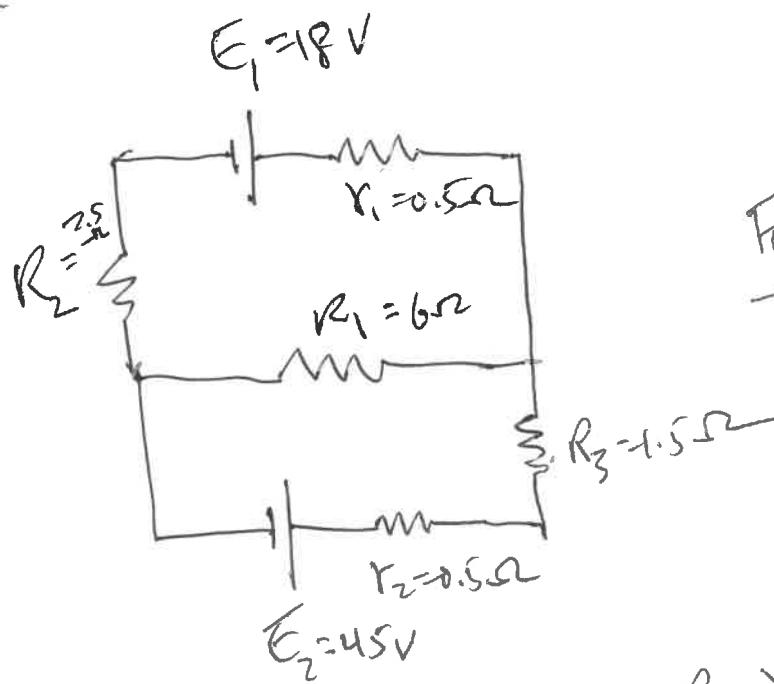


9/21/2011
(1:54pm)


Kirchhoff's rules today, (See. Solved) (P.1)
because I did produce the correct
result using the ways I believe to
be correct, why?
→ figure this out!

The Circuit:



Find: I in
each
resistor!
including
its direction

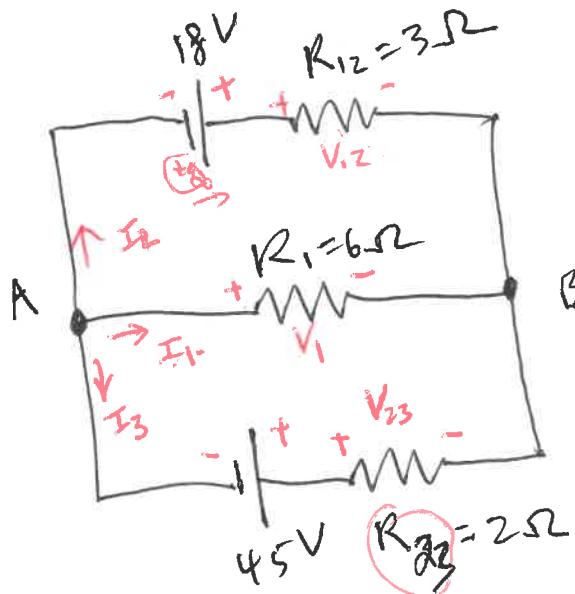Step #1: Simplify the circuit.
R₂ & R₃ in series
R₁ & R₂ in series
i.e. they should draw same current



$$\left\{ \begin{array}{l} R_{12} = R_1 + R_2 \\ R_{23} = R_2 + R_3 \end{array} \right.$$

Step #2: Since we do not know exact current direction before solving the problem.
We can assume the direct of currents

(a) the junction A or node A
Since the direction of currents are assumed, the voltage drop or Voltage difference on each resistor should be consistent to the assumed the current direction!

Step #3: Apply Kirchhoff's rule

Ohm's Law

$$\left\{ \begin{array}{l} V_{12} = I_2 R_{12} = 3I_2 \\ V_1 = I_1 R_1 = 6I_1 \\ V_{23} = I_3 R_{23} = 2I_3 \end{array} \right.$$

4/21/2011

P.3

@ junction A, no charge accumulation
(build-up)

$I_{out \rightarrow A} \rightarrow " - "$
 $I_{in \rightarrow A} \rightarrow " + "$ current

$$\rightarrow -I_2 - I_1 - I_3 = 0 \quad \dots \quad (1)$$

for

Q up loop: $q_{60} \rightarrow$ "use ~~the~~ e-potential gain"



$$18 - V_{12} + V_1 = 0$$

$$18 - 3I_2 + 6I_1 = 0 \quad \dots \quad (2)$$

could "use the work e-force done"

Q low loop:

$$45 - V_{23} + V_1 = 0$$

$$45 - 2I_3 + 6I_1 = 0 \quad \dots \quad (3)$$

replace I_3 in (3) using (1) $I_3 = -I_2 - I_1$

$$45 - 2(-I_2 - I_1) + 6I_1 = 0$$

$$45 + 2I_2 + 2I_1 + 6I_1 = 0$$

$$2I_2 + 8I_1 = -45 \quad \dots \quad (3)$$

9/21/2011

(P.4)

Rewrite ② & ③

$$\left\{ \begin{array}{l} -3I_2 + 6I_1 = -18 \quad (2) \\ 2I_2 + 8I_1 = -45 \quad (3) \end{array} \right.$$

$$\left\{ \begin{array}{l} -6I_2 + 12I_1 = -36 \quad (2) \\ 6I_2 + 24I_1 = -45 \times 3 \quad (3) \end{array} \right.$$

$$② + ③ \rightarrow 36I_1 = -36 - 135 = -171$$

$$\rightarrow I_1 = -\frac{171}{36} = -4.75 \text{ A}$$

$$I_1 = -4.75 \text{ A} \rightarrow ③ :$$

$$2I_2 + 8(-4.75) = -45$$

$$2I_2 + -38 = -45$$

$$2I_2 = -45 + 38 = -7$$

$$\rightarrow I_2 = -7/2 = -3.5 \text{ A}$$

Finally : $I_3 = -I_1 - I_2 = -(-4.75) - (-3.5)$
 $= 8.25 \text{ A}$